
Setup and compute model

```
close all;

% constants
R = 1000; %resistance
C = 1*10^-6; %capacitance
endT = 5.5*10^-3;
tao = R*C;

%interval of discrete time steps
h = tao*0.1; %time steps must be <= tao to produce an accurate model
h_ = 8*10^-4;

steps = fix(endT/h);
steps_ = fix(endT/h_);

% calculate prediction with time steps of h
Vin = ones(1, steps);
Vc = circuitA(Vin, h, R, C);

% calculate prediction with time steps of h_
Vin = ones(1, steps_);
Vc_ = circuitA(Vin, h_, R, C);
```

Plot model

```
figure();
hold on;
%plot the input voltage
yline(Vin(1), 'b', 'linewidth', 2);
%plot the voltage across the capacitor with time steps of h
plot([0:steps-1]*h, Vc, 'linewidth', 2);
%plot the voltage across the capacitor with time steps of h_
plot([0:steps_-1]*h_, Vc_, 'linewidth', 2);


%plot theoretical charging curve
syms t;
V_out(t) = (1-exp(-t/(R*C)));
fplot(@(t) V_out(t), [0 endT], 'linewidth', 2);

%plot tao
xline(tao, 'linewidth', 2);

set(gca, 'linewidth', 2);
set(gca, 'fontsize', 14);
xlabel("Time (s)")
ylabel("Voltage (V)");
legend("V_{in}", "V_{out}", "V'_{out}", "V_c(t)", "RC time constant", ...
       'Location','southeast');
title("Charging curves for capacitor in circuit A");
```

```
hold off;  
exportgraphics(gca, "chargingCurves.eps", "Resolution", 300);
```

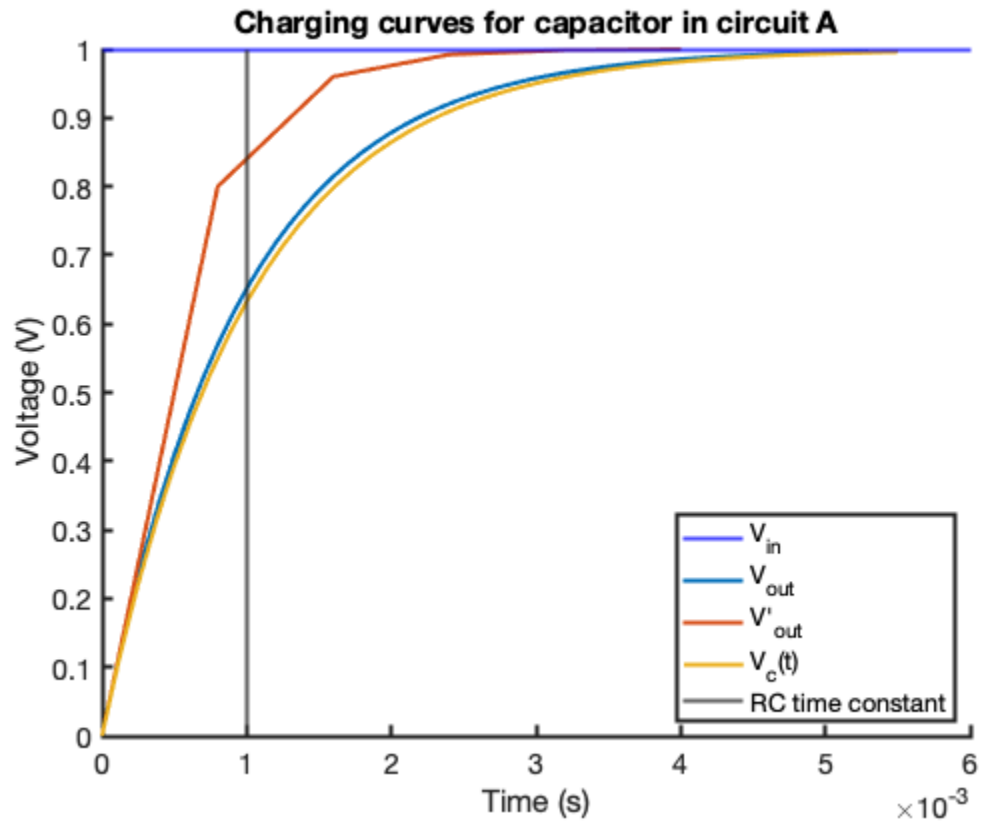Warning: Exported image displays axes toolbar. To remove axes toolbar from image, export again.



Published with MATLAB® R2020a